

FM Transmitter

LAB REPORT

Dhanush V Nayak


EE23BTECH11015

Aim: The aim of this experiment is to build FM Transmitter circuit using BC547 Transistor. Also we aim to understand principles of FM modulation.

Components:

- 1) Condenser Mic
- 2) BC547 Transistor
- 3) Antenna (Single Stranded Wire)
- 4) $0.22\mu H$ inductor
- 5) 330Ω and $4.7k\Omega$ resistor

Circuit Diagram

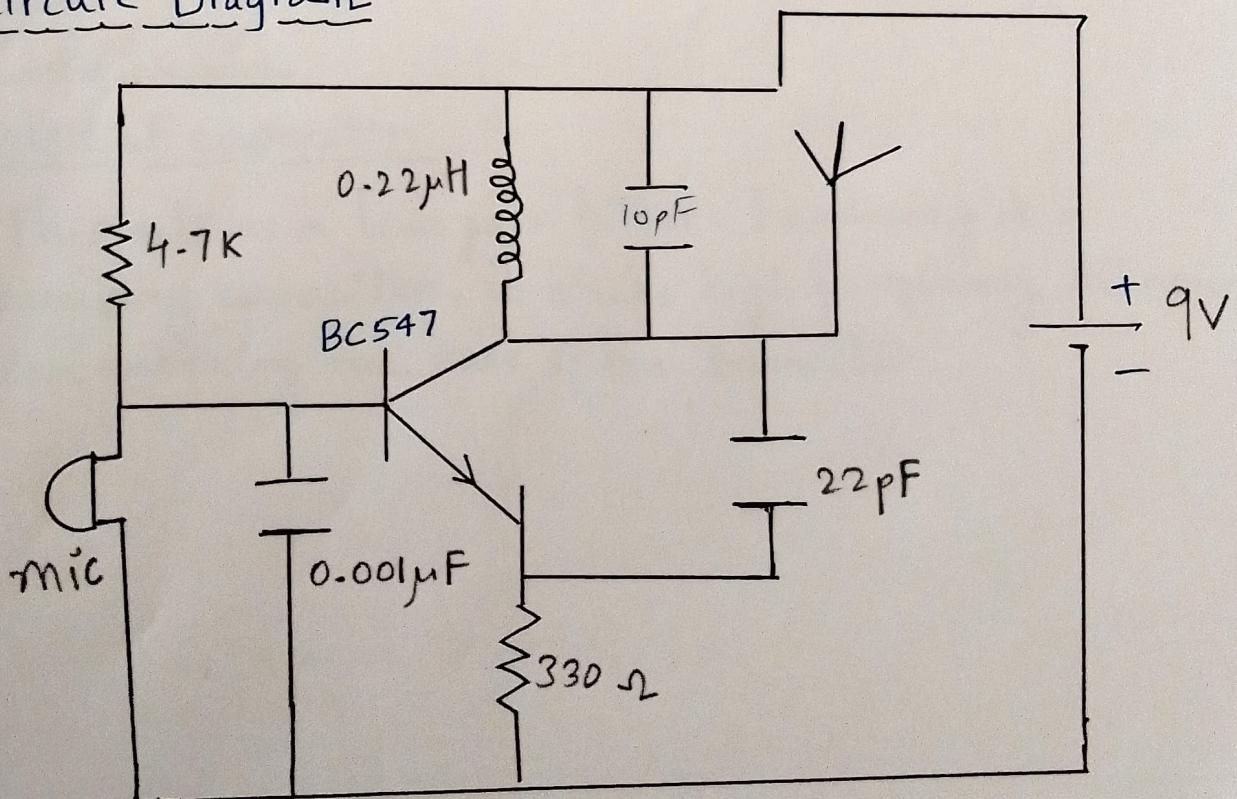

Working:

1) Tap Microphone

It works on the principle of piezoelectric effect. Therefore when we tap microphone, it converts the mechanical stress/energy into electric signal.

- This signal represents the sound of the tap and is typically in form of rapid oscillations of voltage.

2) Base Band Signal Processing

- AC signal from the microphone is sent to the base terminal of the transistor BC547.
- This signal represents our baseband signal.


3) Capacitors

0.001 μ F capacitor

- This acts as a low pass filter. Functioning as a decoupling capacitor, it blocks high frequency AC noises from entering the base of the transistor.

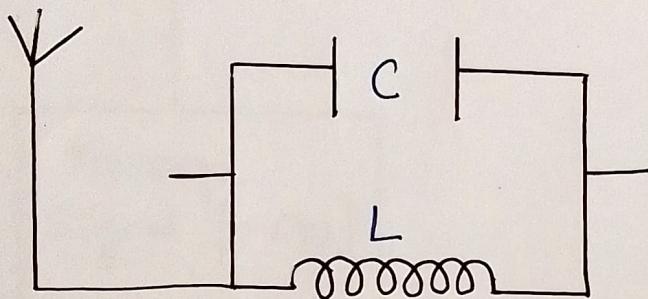4) LC Tank Circuit


- The Tank Circuit consists of the inductor and a ceramic capacitor. It acts like a electric resonator.
- This part of circuit is responsible for generating carrier frequency.



$$f = \frac{1}{2\pi\sqrt{LC}}$$

- When the circuit is powered on, current oscillates back and forth between inductor and capacitor at this resonant frequency.
- Here the capacitor should not be electrolytic as both sides of the capacitor the charging should take place. If we use electrolytic capacitor, the leads get polarised.
- The transistor here amplifies the weak audio signals. The amplified audio signal is coupled and circuit oscillates at its resonant frequency.
- The antenna radiates the modulated FM signal as radio waves.

FM Modulation:

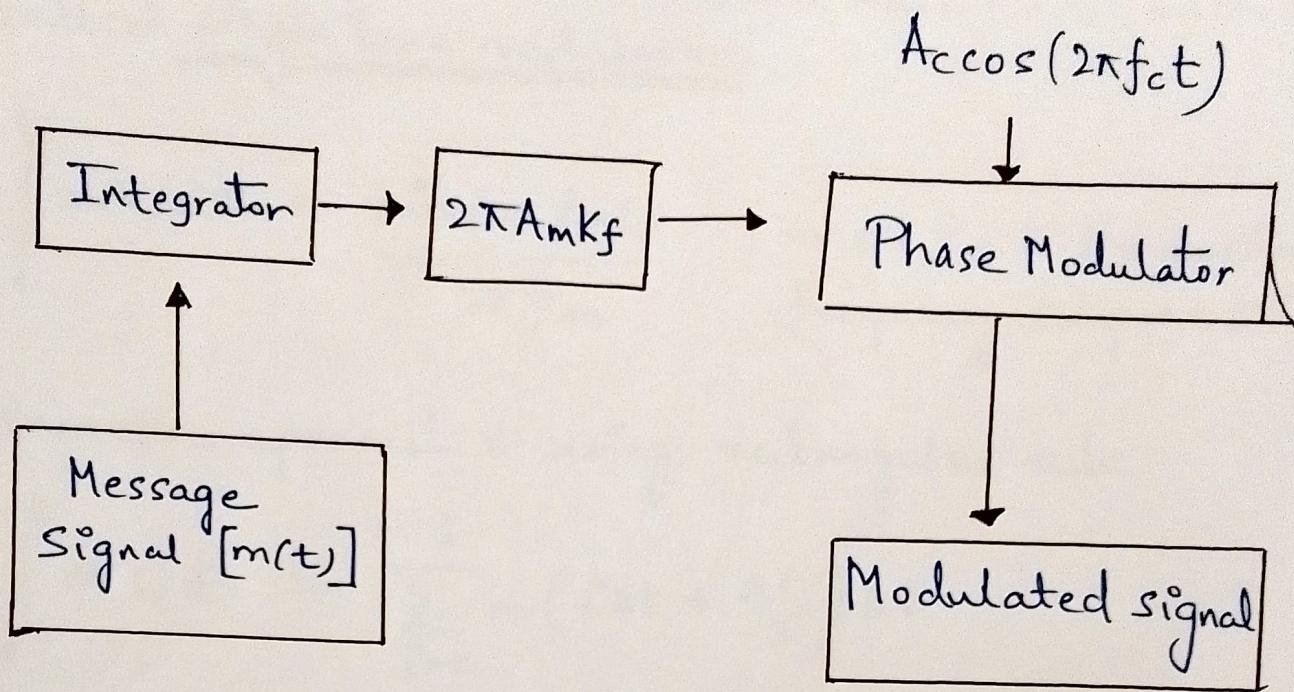

A_m → amplitude of modulating signal

K_f → sensitivity of frequency modulator

f_c → carrier frequency.

Modulated signal is given by :

$$y(t) = A_c \cos \left(2\pi f_c t + 2\pi f_\Delta \int_0^t m(\tau) d\tau \right)$$

$$f_\Delta = A_m K_f$$

where f_Δ is the frequency deviation.

From computation perspective the baseband signal can be approximated as a sinusoidal wave. This method is called single tone modulation.

$$\int_0^t m(\tau) d\tau = \frac{\sin(2\pi f_m t)}{2\pi f_m} ; \text{ where } f_m \text{ is the maximum frequency component.}$$

alternative approach is using rectangular rule.

$$\int_0^t m(\tau) d\tau = \sum_{i=0}^{N-1} m\left(i\Delta t + \frac{\Delta t}{2}\right) \Delta t$$

$$N \rightarrow \text{number of intervals} ; \quad \Delta t = t/N \rightarrow \text{time step}$$

Using these techniques:

$$y(t) = A_c \cos\left(2\pi f_c t + 2\pi A_c K_f \cdot \sum_{i=0}^{N-1} m\left(i\Delta t + \frac{\Delta t}{2}\right) \Delta t\right)$$

Carson's Rule states that nearly 98% of the power of a frequency-modulated signals lies in its Bandwidth.

Consider computing fourier transform of $y(t)$; using DFT.

$$Y(k) = \sum_{n=0}^{N-1} y(n) e^{-j2\pi kn/N}$$

Power Spectral Density :

$$PSD = |Y(k)|^2$$

After computing PSD of modulated signal; we apply a masking function for better results and accuracy of spectral density .


Masking Function ; it's like creating a threshold and selecting frequencies above it.

$$\text{Modulation Index : } \rightarrow h = \frac{\Delta f}{f_m}$$

$h \ll 1$; narrow band FM


$h \gg 1$; wideband FM


Sample input signal .(mct)

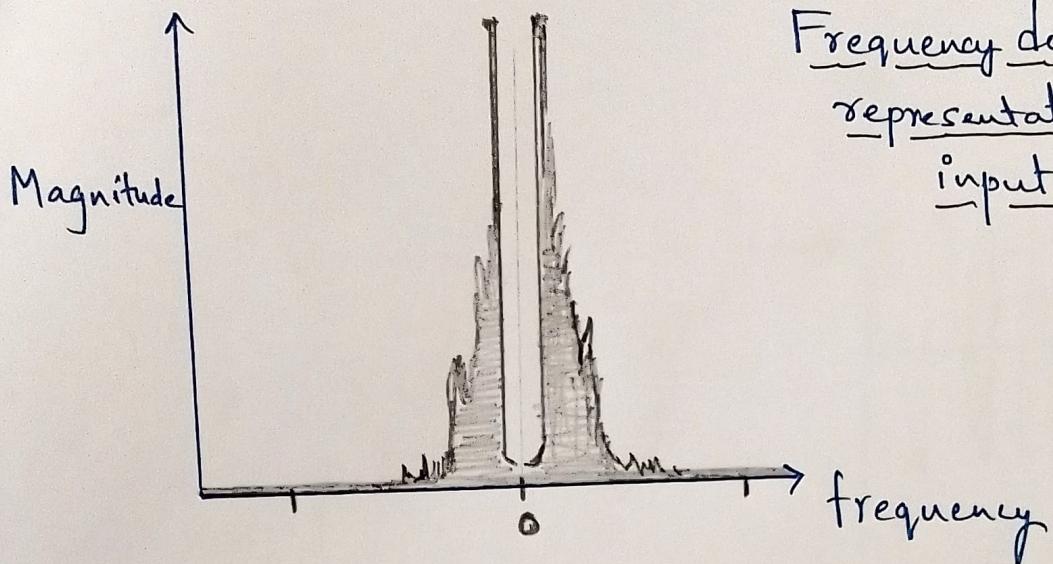

Frequency domain
representation of
input signal.

$Y(k)$ representation .

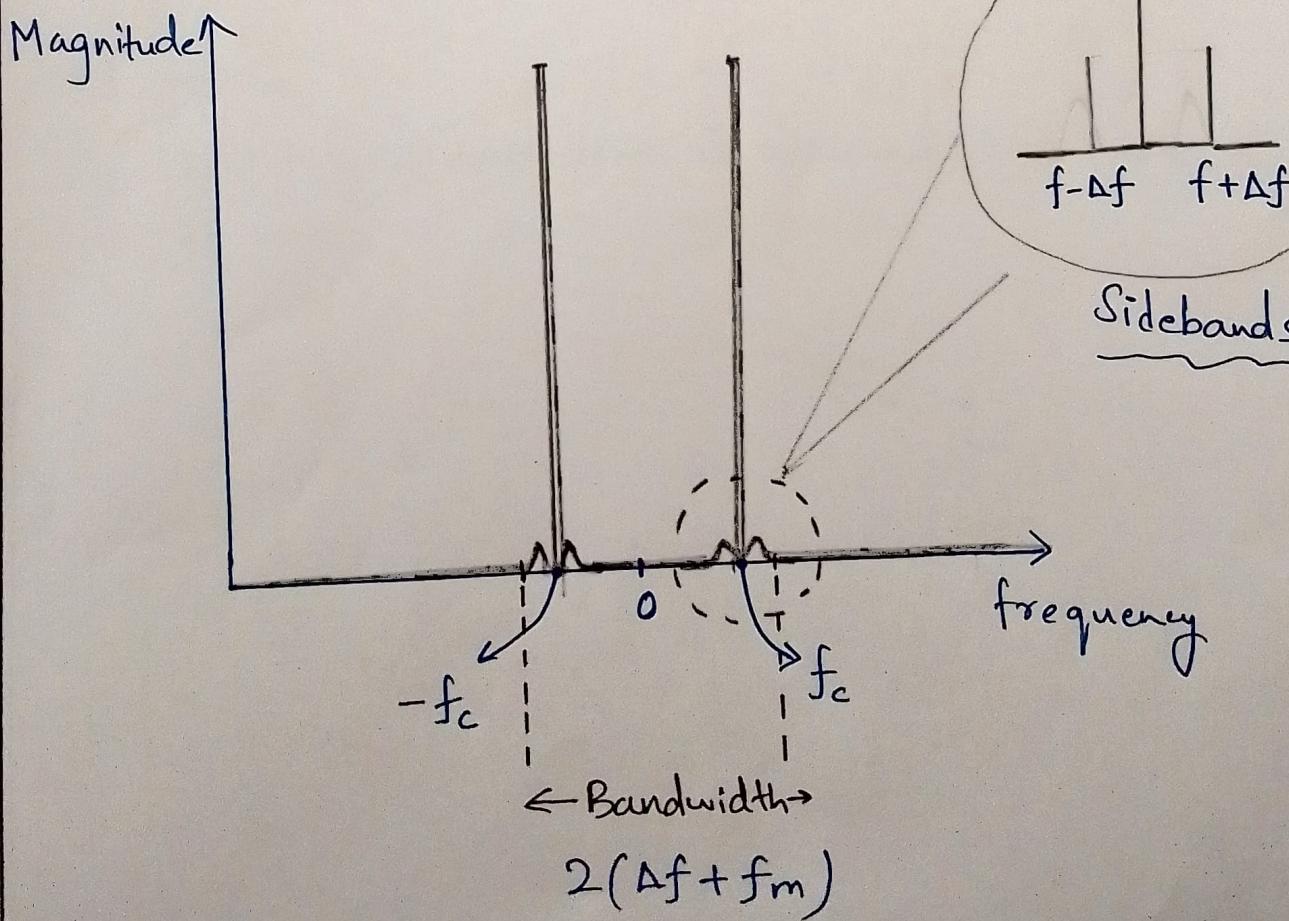


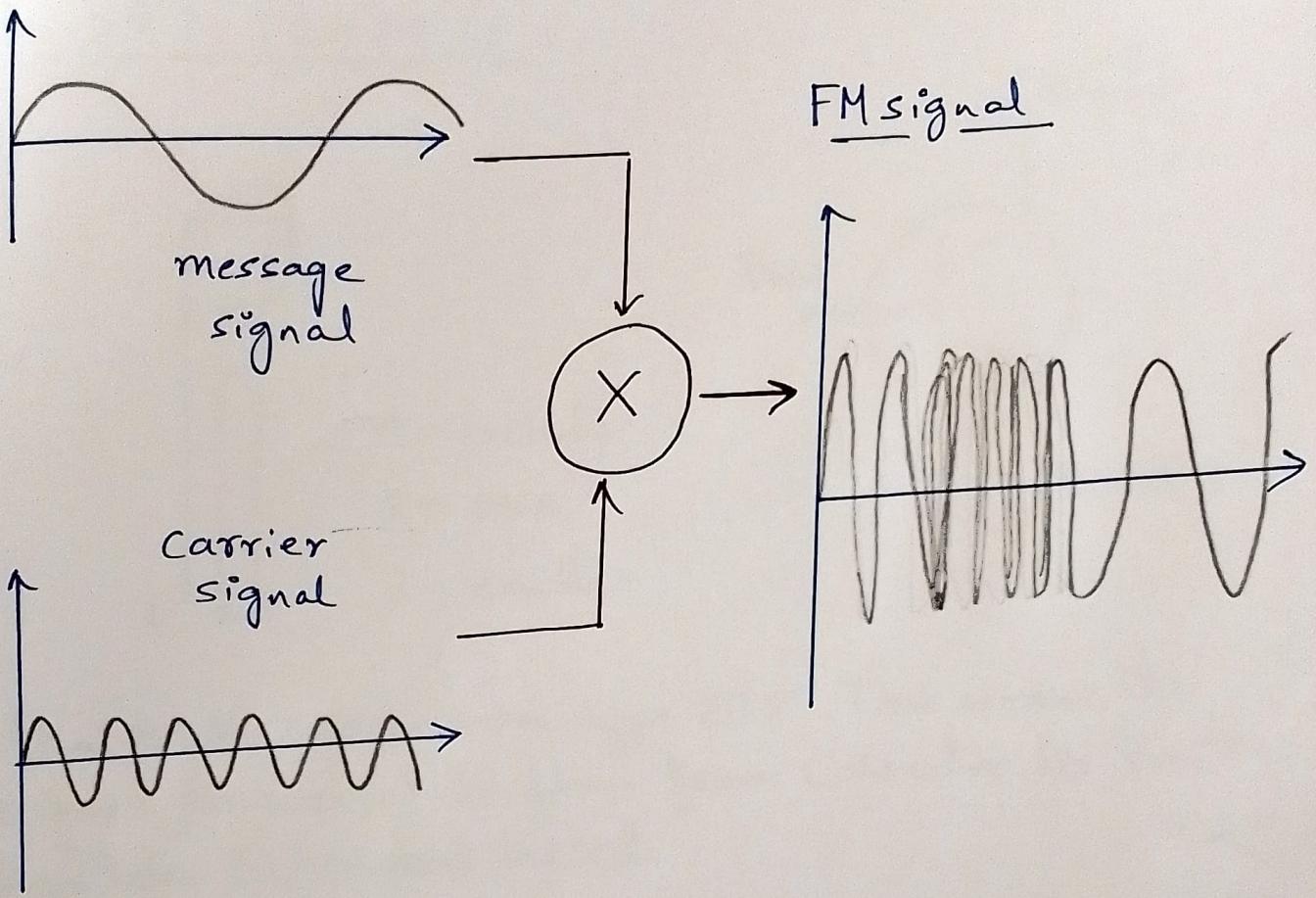


Observations:

The frequency transmission is observed at a frequency 97.3 MHz.

BC 547 Transistor

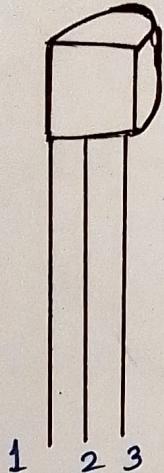

1 - collector
2 - base
3 - emitter

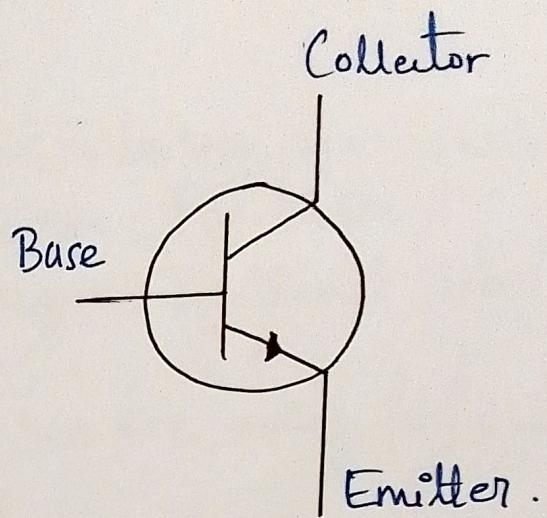

- The BC547 is an NPN type BJT. This means it's designed for current to flow from Collector to Emitter when base is forward biased.
- When a positive voltage is applied to base relative to emitter the base-emitter junction the base-emitter junction becomes forward biased. This allows majority charge carriers from emitter to flow into base region.
- Even though base current is small due to thin base region, it creates strong electric field. The field significantly affects the depletion region around base-collector junction.

Precautions

- 1) Placement and Orientation of the antenna are crucial for optimal transmission performance. For better transmission make sure that length is atleast $\lambda/4$.
- 2) Ensure that the power supply we are using for circuit should be stable and regulated.
- 3) Make sure to use less number of connecting wires to prevent noise.

Conclusion :

We were successfully able to demonstrate the working of FM Transmitter. The bandwidth of the transmitted signal can be modified by changing or make some changes in the tank circuit.